

# Chapter 5. Fast Addition (Part 1)

---

Contents (Part 1):

- 1. Full Adder**
- 2. Ripple-Carry Adder**
- 3. Carry-Lookahead Adder**

Contents (Part 2)


- 4. Conditional Sum Adder**
- 5. Manchester Adder**
- 6. Carry Select Adder**
- 7. Carry Skip Adder**
- 8. Carry Save Adder**

# Single-digit Adder

---
 
## 1. Consider adding two decimal digits

- $s = x + y$ , where  $x$ ,  $y$ , and  $s$  are single digit numbers.
- There is also a carry-in  $c_{in}$  and a carry-out  $c_{out}$ .




## 2. Can you write $s$ and $c_{out}$ as functions of $x$ , $y$ , and $c_{in}$ ?

# Full Adder

---

 1. Now consider designing a one-bit adder (full adder):
  - $S = x + y$ , where  $x$  and  $y$  are one-bit operands,  $s$  one-bit sum.
  - There is also one-bit carry-in  $c_{in}$  and one-bit carry-out  $c_{out}$ .




# Full Adder

---
 
## 2. Arithmetic equations for one-bit adder:

- $s = (x + y + c_{in}) \bmod 2$ , and  $c_{out} = [(x + y + c_{in}) / 2]$ .



## 3. What are the logic equations for the full adder?

# Full Adder

---

4. Recall how to design a circuit for this as a digital logic design problem:
  - 1) create a truth table
  - 2) write Karnaugh map
  - 3) optimise Karnaugh map
  - 4) obtain logic equation
  - 5) draw the circuit

# Full Adder

---

- Arithmetic equations:

- $S = (X + Y + C_{in}) \bmod 2$ , and  $C_{out} = [(X + Y + C_{in}) / 2]$ .

- Truth table:

X	Y	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

- Logic equations: (Karnaugh map step omitted)

- $S = X \oplus Y \oplus C_{in}$ ,  $C_{out} = XY + C_{in}(X \oplus Y)$

# Full Adder

## 1. Representation of the inputs and outputs:

- Input:  $X$ ,  $Y$ ,  $C_{in}$  and Output:  $S$ ,  $C_{out}$
- All are one-bit binary numbers


## 2. Output logic functions:

- $S = X \oplus Y \oplus C_{in}$ ,  $C_{out} = XY + C_{in}(X \oplus Y)$
- $S$  is the sum bit, and  $C_{out}$  is the carry-out bit.

## 3. Circuit diagram for the 1-bit adder shown:

 
## 4. Space complexity (C) and critical path delay (T):

- $C = 2 \text{ AND} + 1 \text{ OR} + 2 \text{ XOR}$ 
  - 5 gates in total.
- Critical path delay?


 
# Critical Path Delay for Full Adder


- First to find the critical path:
  - $X/Y \rightarrow$  (red dashed line)  $\rightarrow C_{out}$
- Then find its delay
  - $T = 3 \Delta_G$





# Finding Critical Path (cp)

Input	Output	Delay
X/Y	S	$2\Delta_G$
X/Y	$C_{out}$	$3\Delta_G \rightarrow \text{cp}$
$C_{in}$	S	$\Delta_G$
$C_{in}$	$C_{out}$	$2\Delta_G$

 


- Next we will show how to use FA as building blocks to make ripple-carry adder.

# Ripple Carry Adder: 4-bit RCA

## 1. Algorithm for 1-bit addition:

- $S_i = X_i \oplus Y_i \oplus C_i, \quad C_{i+1} = X_i Y_i + C_i(X_i \oplus Y_i), i=0,1,2,3.$

 
## 2. Circuit for the 4-bit ripple carry adder:



## 3. Complexities:

- $C = 4 \text{ FA} = 8\text{AND} + 4\text{OR} + 8\text{XOR}$
- What is its critical path delay?

# Ripple Carry Adder: 4-bit RCA

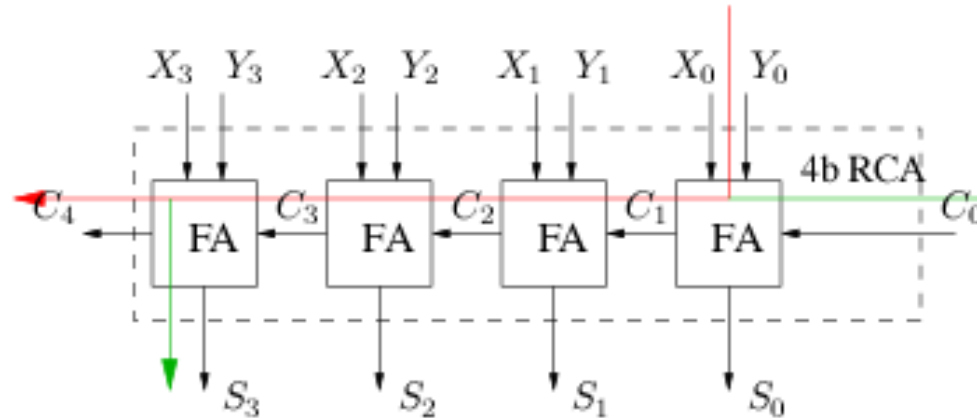

- Critical path (depending on the delay table for FA)
  - $X_0/Y_0 \rightarrow C_1 \rightarrow C_2 \rightarrow C_3 \rightarrow C_4$
- Critical path delay
  - $T = 3\Delta_G + 2\Delta_G + 2\Delta_G + 2\Delta_G = 9\Delta_G$
  - Or,  $T = 4\Delta_{FA} = 8\Delta_G$  (as in textbook)
  - why different?

# FA and RCA: alternate design

## 1. Algorithm for FA:

- $S = X \oplus Y \oplus C_{in}$ ,  $C_{out} = XY + C_{in}X + C_{in}Y$

## 2. Circuit complexity and critical path delay for FA:

- $C = 3 \text{ AND} + 1 \text{ OR} + 2 \text{ XOR}$


- 6 gates in total.

- $T = 2\Delta_G$

## 3. A 4-bit RCA built with this FA:

- $C = 4 \text{ FA} = 12\text{AND} + 4\text{OR} + 8\text{XOR}$

- $T = 8\Delta_G$

 


# Ripple Carry Adder Complexities

---

- 4-bit RCA:
  - Circuit complexity
    - 4 FA:
  - Critical path delay:
    - $4\Delta_{\text{FA}} = 8\Delta_{\text{G}}$
- $n$ -bit RCA:
  - Circuit complexity
    - $n$  FA:
  - Critical path delay:
    - $n\Delta_{\text{FA}} = 2n\Delta_{\text{G}} \rightarrow O(n)$
- RCA is the simplest and also the slowest adder.
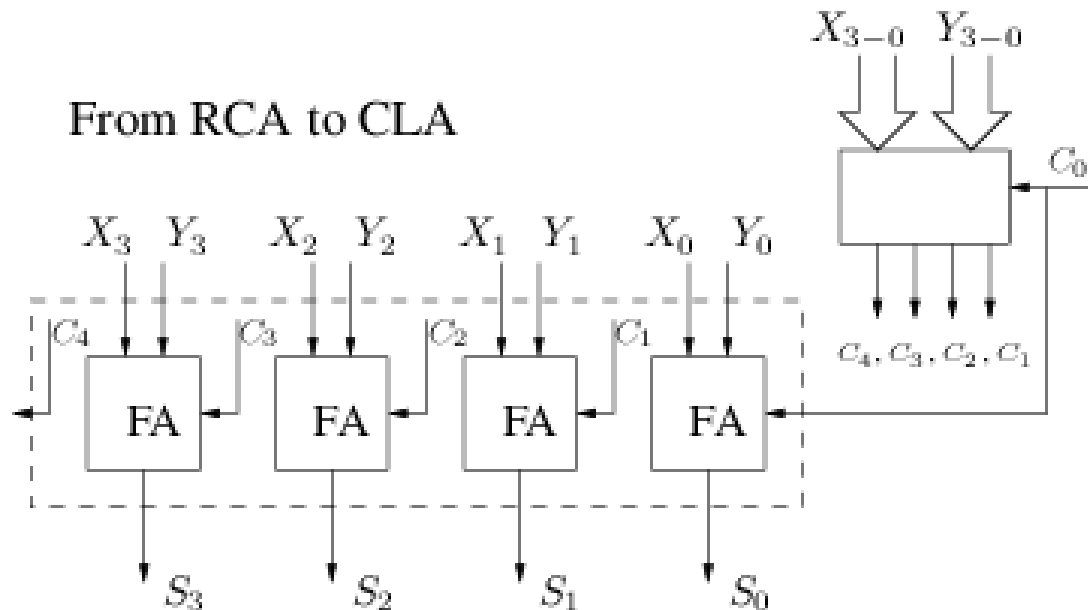
# To Speed up RCA

- Idea:
  - In order to cut off the carry chain, the carries  $c_i$  are generated separately.



# Carry-Lookahead Addition

---


- $\rightarrow$  Let  $\begin{cases} G_i = x_i y_i \\ P_i = x_i \oplus y_i \end{cases}$  for  $i = 0, 1, 2, 3$ . (1)

$$\rightarrow \text{Then } \begin{cases} c_1 = G_0 + c_0 P_0 \\ c_2 = G_1 + c_1 P_1 = G_1 + G_0 P_1 + c_0 P_0 P_1 \\ c_3 = G_2 + G_1 P_2 + G_0 P_1 P_2 + c_0 P_0 P_1 P_2 \\ c_4 = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + c_0 P_0 P_1 P_2 P_3 \end{cases} \quad (2)$$

$$\rightarrow \text{And } S_i = x_i \oplus y_i \oplus c_i \text{ for } i = 0, 1, 2, 3. \quad (3)$$

# Carry-Lookahead Adder


- Circuit Diagram

 



# Carry-Lookahead Adder: Delay

- Critical Path Delay:

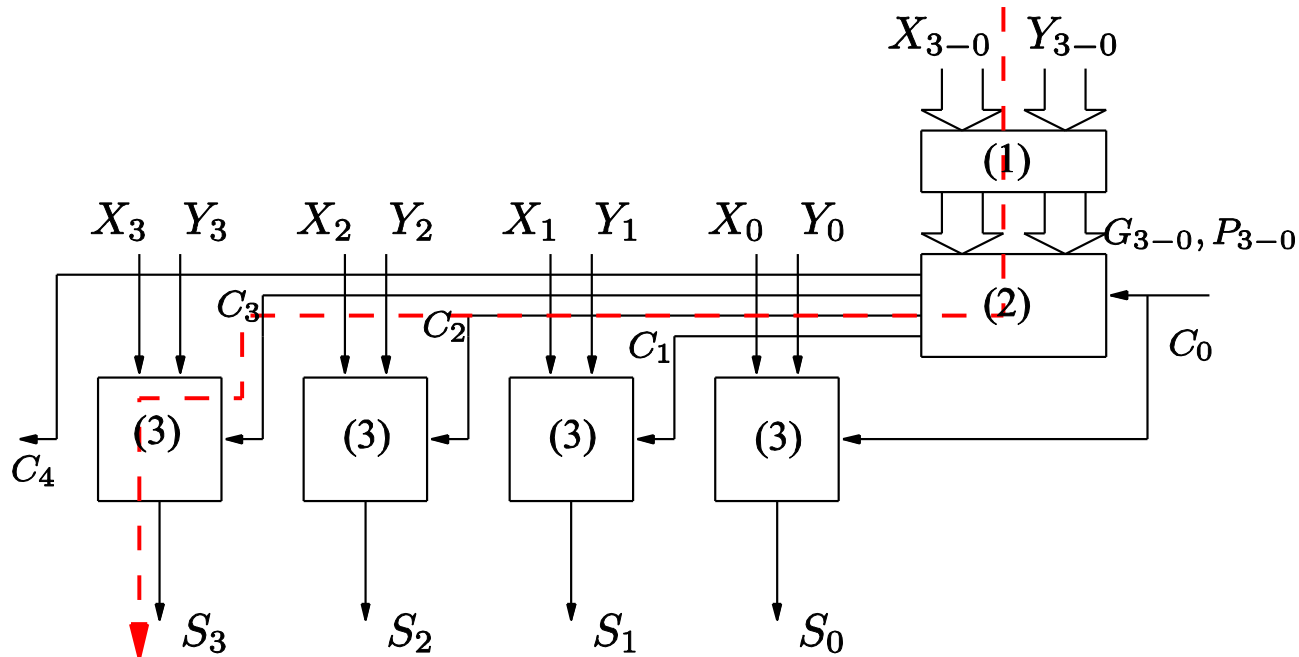


- $T = 1\Delta_G + 2\Delta_G + 1\Delta_G = 4\Delta_G$  ✓
- $T = 1\Delta_G + 2\Delta_G + 2\Delta_G = 5\Delta_G$  (textbook)

# Construction of n-bit CLA

- ➔ Change equation (3) into

$$\text{And } S_i = P_i \oplus c_i \text{ for } i = 0, 1, 2, 3. \quad (3)$$


- ➔ 4-bit CLA diagram can be shown as

 
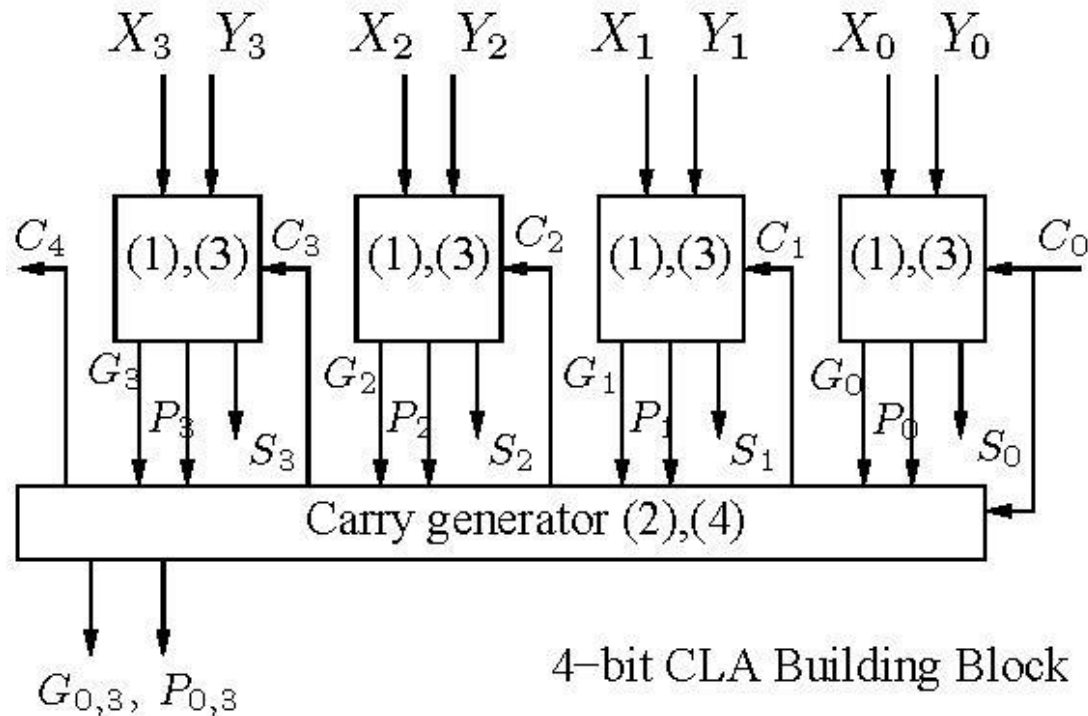
# 4-bit CLA Building Block


- ➔ Let 
$$\begin{cases} G_{0,3} = G_3 + G_2P_3 + G_1P_2P_3 + G_0P_1P_2P_3 \\ P_{0,3} = P_0P_1P_2P_3 \end{cases} \quad (4)$$

➔ Then a 4-bit CLA building block can be shown as


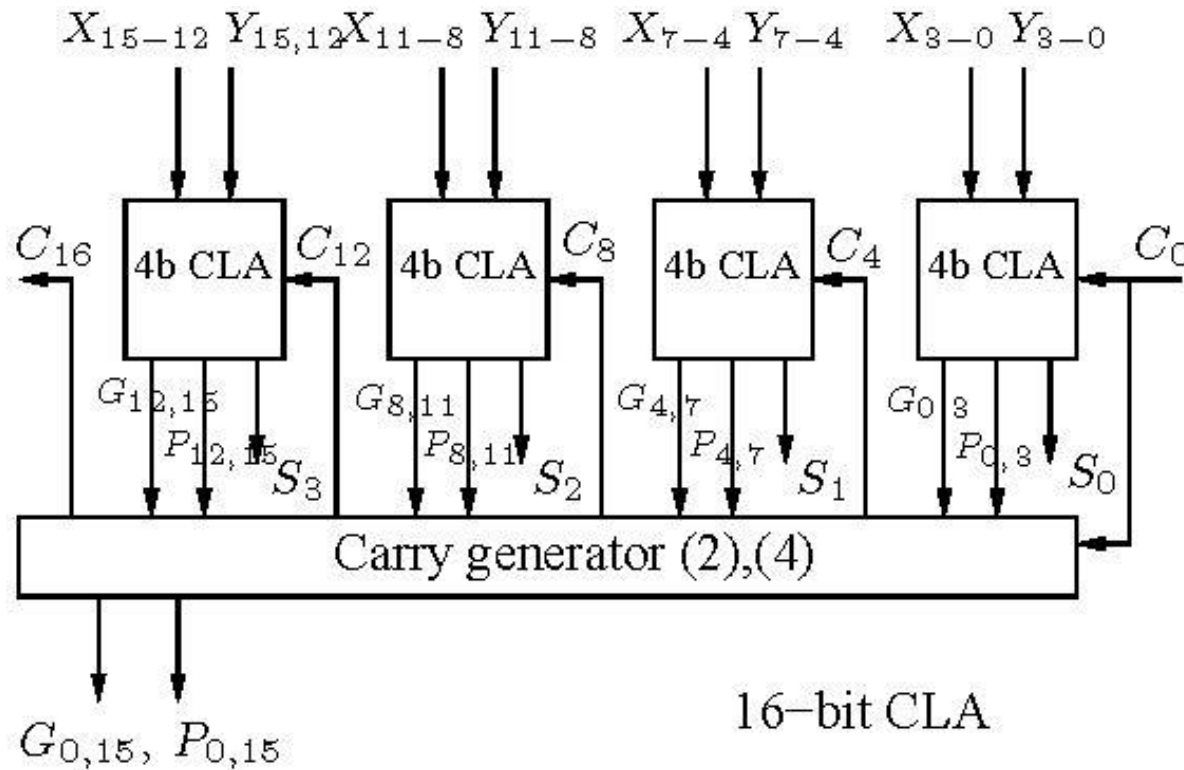
# 16-bit CLA Using 4-bit CLA Blocks

- Circuit diagram for 16-bit CLA built with 4-bit CLA blocks
  - (Two-level carry lookahead structure)



# 16-bit CLA Using 4-bit CLA Blocks

- The carry generator module is the same as that in 4-bit CLA,
- where equation (2) becomes

$$\begin{cases} c_4 = G_{0,3} + c_0 P_{0,3} \\ c_8 = G_{4,7} + c_4 P_{4,7} = G_{4,7} + G_{0,3} P_{4,7} + c_0 P_{0,3} P_{4,7} \\ c_{12} = G_{8,11} + G_{4,7} P_{8,11} + G_{0,3} P_{4,7} P_{8,11} + c_0 P_{0,3} P_{4,7} P_{8,11} \\ c_{16} = G_{12,15} + G_{8,11} P_{12,15} + G_{4,7} P_{8,11} P_{12,15} + G_{0,3} P_{4,7} P_{8,11} P_{12,15} + c_0 P_{0,3} P_{4,7} P_{8,11} P_{12,15} \end{cases} \quad (5)$$

- And equation (4) becomes

$$\begin{cases} G_{0,15} = G_{12,15} + G_{8,11} P_{12,15} + G_{4,7} P_{8,11} P_{12,15} + G_{0,3} P_{4,7} P_{8,11} P_{12,15} \\ P_{0,15} = P_{0,3} P_{4,7} P_{8,11} P_{12,15} \end{cases} \quad (6)$$

- Note that eqn (5) can be realized using the same logic for eqn (2), Page 10.
- And eqn (6) can be realized using the same logic as for eqn (4), Page 14.

# 16-bit CLA

---

- Circuit complexity:
  - Four 4-bit CLA plus a carry generator module.
- Critical Path Delay:
  - $T = 8\Delta_G$ , or  $T = 9\Delta_G$  as given in the textbook
  - Both the above results are considered as correct.

# n-bit CLA

---

- 64-bit CLA
  - Circuit complexity: four 16-bit CLA plus a carry generator
  - Critical path delay:  $12 \Delta_G$
- Delay for n-bit CLA built in this way:
  - $T = 4 \log_4 n \Delta_G$
  - or  $T = (4 \log_4 n + 1) \Delta_G$  as given in the textbook