

Final Examination

ELEC8550 Computer Arithmetic, Fall 2020

December 12, 2020

Read before start writing your solution	
1.	It is an open book examination. There are five problems.
2.	The exam time is 125 minutes (7:00pm-9:05pm) which includes the time it takes you to open the exam problem file from mailbox and answer the problems.
3.	Write down ❶ <u>your name</u> , ❷ <u>ID</u> and ❸ <u>page number</u> at the top of each page of your answer sheets.
4.	A 15-minute time span at 9:05pm-9:20pm will be available to you to scan your answer sheets, form one pdf file and upload the file to Resources/Online exams/final exam at Blackboard course website.
5.	In order to minimize the geometric distortion and unrecognizability caused by photo-taking, your answer sheets must be scanned (using either a scanner or software based) and then formed into <i>one pdf file</i> . There will be 10% deduction for failing to do so.
6.	The deadline that your submitted answer file will appear at Blackboard is 9:20pm.
7.	Submission later than 9:20pm but before 9:30pm will be deducted 10%. Submission after 9:30pm will be assigned zero mark.
8.	The use of external aid of any kind is not permitted. Certain measures will be taken if plagiarism is found. You are expected to take this final exam fairly.

Problem 1

$$\begin{aligned} \text{Answer)} \quad -0.8_{10} &= \left(-\frac{8}{10}\right)_{10} = -[(8)_{10} \times (0.1)_{10}] = -[(1000)_2 \times (0.5)_{10} + (0.5)_{10}] \\ &= -[(1000)_2 \times \{(0.1)_2 + (0.1)_2\}] \\ &= -[(1000)_2 \times (0.0011)_2] \\ &= (-1)^4 [1.0 \times 2^3] \end{aligned}$$

$$F_1 = 1.0 \times 2^3 = 1.0 \times 2^{130-127}$$

$$F_2 = (-1)^1 \times 1.10011 \times 2^{-4} = (-1)^1 \times 1.10011 \times 2^{123-127}$$

$$\begin{aligned} \Rightarrow F_3 = F_1 \times F_2 &= (-1)^1 \times (1.0 \times 1.10011) \times 2^{(130-127+123)-127} \\ &= (-1)^1 \times 1.10011 \times 2^{126-127} \end{aligned}$$

\therefore IEEE 64-bit representation that consists of sign, ^{exponent} ~~magnitude~~ & significand is as follows:

$$s = 1$$

$$e = 1111 \ 1110$$

$$f = 10011001100110011001100$$

Problem 2

$$\text{Answer)} \quad y = [x] ; \quad x = x_1 x_0 . x_{-1} x_{-2} ; \quad y = y_2 y_1 y_0$$

x_1	x_0	x_{-1}	x_{-2}	y $\{y_2 y_1 y_0\}$	Error = $y - x$
0	0	0	0	000	+0
0	0	0	1	001	+3/4
0	0	1	0	001	+1/2
0	0	1	1	001	+1/4
0	1	0	0	001	+0
0	1	0	1	010	+3/4
0	1	1	0	010	+1/2
0	1	1	1	010	+1/4
1	0	0	0	010	+0
1	0	0	1	011	+3/4
1	0	1	0	011	+1/2

x_2	x_0	x_{-1}	x_{-2}	y {0, 1, 2, 3}	Error = $y - x$
1	0	1	1	011	+1/4
1	1	0	0	011	+0
1	1	0	1	100	+3/4
1	1	1	0	100	+1/2
1	1	1	1	100	+1/4

∴, Maximal errors, $e_{\max}^+ = +3/4$

$$\text{Bias} = \frac{1}{16} [4(+\frac{1}{4} + \frac{1}{2} + \frac{3}{4})] = \frac{3/2}{4} = +\frac{3}{8}$$

For y_0

x_2, x_0	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	1	0	0	0
10	0	1	1	1

$$\begin{aligned} y_0 &= \bar{x}_0 x_{-2} + \bar{x}_0 x_{-1} + x_0 \bar{x}_{-1} \bar{x}_{-2} \\ &= \bar{x}_0 (x_{-1} + x_{-2}) + x_0 (\bar{x}_{-1} \cdot \bar{x}_{-2}) \\ &= \bar{x}_0 (x_{-1} + x_{-2}) + x_0 (\overline{x_{-1} + x_{-2}}) \\ &= x_0 \oplus (\overline{x_{-1} + x_{-2}}) \end{aligned}$$

For y_1



x_2, x_0	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	1	0	0	0
10	1	1	1	1

$$\begin{aligned} y_1 &= x_1 \bar{x}_0 + x_1 (\bar{x}_{-1} \cdot \bar{x}_{-2}) + \bar{x}_1 x_0 x_{-2} + \bar{x}_1 x_0 x_{-1} \\ &= x_1 (\bar{x}_0 + \bar{x}_{-1} \bar{x}_{-2}) + \bar{x}_1 x_0 (x_{-2} + x_{-1}) \\ &= x_1 (\overline{x_0 \cdot (x_{-1} + x_{-2})}) + \bar{x}_1 (x_0 \cdot (x_{-2} + x_{-1})) \\ &= x_1 \oplus (x_0 \cdot (x_{-1} + x_{-2})) \end{aligned}$$

For y_2


x_2, x_0	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	1	1	1
10	0	1	1	1

$$y_2 = x_1 x_0 (x_{-1} + x_{-2})$$

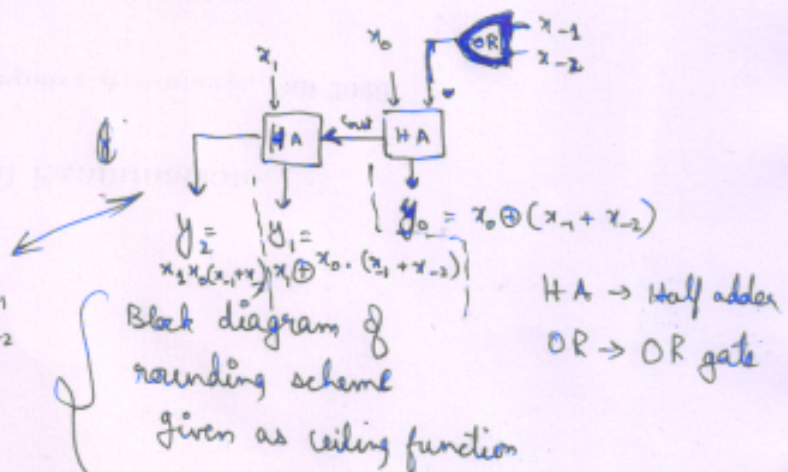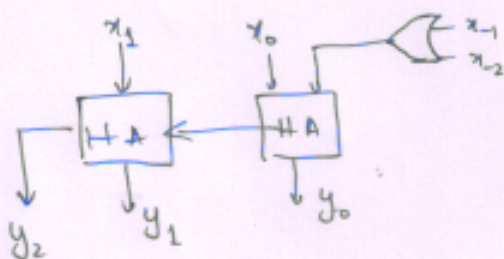

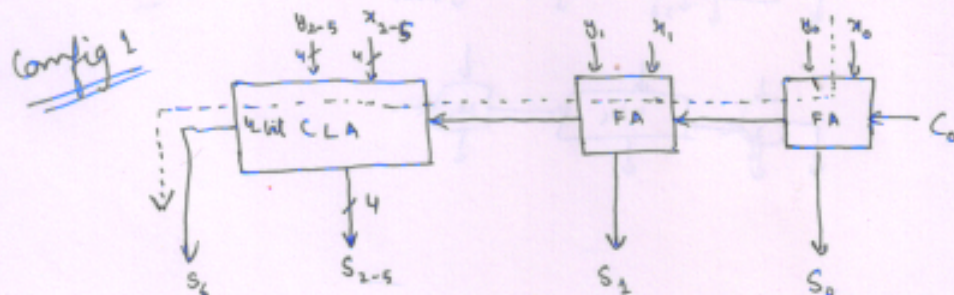Problem 3)


Answer) For the following configuration of the CLA and the two Full Adders, the critical path delay will be minimal




$$\begin{aligned} \text{critical path delay of 6-bit adder} &= T_{x/y \rightarrow \text{Carry}}^{\text{FA}} + T_{\text{cin} \rightarrow \text{Carry}}^{\text{FA}} + T_{C_0 \rightarrow C_4}^{\text{CLA}} \\ &= 2\Delta_G + 2\Delta_G + 4\Delta_G \end{aligned}$$

$$\text{Minimal critical path delay} = \boxed{8\Delta_G}$$

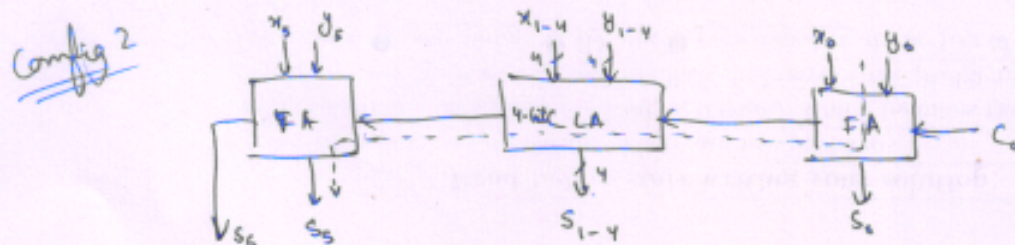Other configurations that are possible are


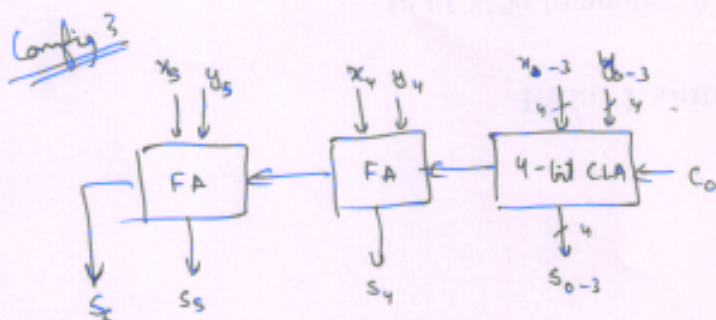
$$\begin{aligned} T_{\text{critical}} &= T_{x/y \rightarrow \text{Carry}}^{\text{FA}} + T_{C_4 \rightarrow C_1}^{\text{CLA}} + T_{\text{cin} \rightarrow s_0}^{\text{FA}} \\ &= 2\Delta_G + 4\Delta_G + 3\Delta_G = 9\Delta_G \end{aligned}$$



$$\begin{aligned} T_{\text{critical}} &= T_{x/y \rightarrow C_4}^{\text{CLA}} + T_{\text{cin} \rightarrow \text{Carry}}^{\text{FA}} + T_{\text{cin} \rightarrow s}^{\text{FA}} \\ &= 4\Delta_G + 2\Delta_G + 3\Delta_G = 9\Delta_G \end{aligned}$$

∴ Minimal critical path delay = $8\Delta_G$ for config. ①

Problem 4) Designing the 26 bit carry-select adder

⇒ Let 26-bit carry select adder be divided into l groups of length k_1, k_2, \dots, k_l

⇒ $(l-1)2\Delta_g = 2k_l\Delta_g$ (For FA's for addition & assuming i/b's to MUX are available at exactly same time)

$$k_l = l-1 \quad \text{Group sizes are } 1, 1, 2, 3, 4, \dots$$

$$\text{Also, } 1 + \frac{l(l-1)}{2} \geq n \Rightarrow l(l-1) \geq 2n+1 \quad (n=26)$$

$$\Rightarrow l(l-1) \geq 53$$

$$\therefore, l = 8$$

And group size are, $k_1 = 1, k_2 = 1, k_3 = 2, k_4 = 3, k_5 = 4, k_6 = 5, k_7 = 6, k_8 = 4$

$$\therefore, C_{\text{select}} = \text{50 FA's} + 1 \text{ HA}$$

$$T_{\text{select}} = 2\Delta_g + 2 \times 7\Delta_g = 15\Delta_g$$

* Designing the 26-bit carry-skip adder

⇒ Let 26-bit adder be divided into k groups of equal sizes

$$\begin{aligned} T_{\text{carry}} &= (k-1)t_n + t_b + \left(\frac{n}{k} - 2\right)(t_s + t_b) + (k-1)t_n \\ &= \left(4k + \frac{2n}{k} - 7\right)\Delta_g \quad (t_n = 2\Delta_g, t_s = t_b = \Delta_g) \end{aligned}$$

$$\Rightarrow \frac{dT_{\text{carry}}}{dk} = 4 - \frac{2n}{k^2} = 0 \Rightarrow k = \sqrt{\frac{n}{2}} \Rightarrow k = \sqrt{\frac{26}{2}} = \sqrt{13}$$

$$\begin{aligned} T_{\text{opt}} &= \left(4\sqrt{13} + \frac{2(26)}{\sqrt{13}} - 7\right)\Delta_g = \left(\frac{52 + 52 - 7\sqrt{13}}{\sqrt{13}}\right)\Delta_g = \left(\frac{104 - 7\sqrt{13}}{\sqrt{13}}\right)\Delta_g \\ &= 21.8\Delta_g \end{aligned}$$

$$\therefore, C_{\text{skip}} = 26 \text{ FA's}$$


$$T_{\text{skip}} = 21.8\Delta_g$$

Hence, $C_{\text{select}} > C_{\text{skip}}$ & $T_{\text{skip}} > T_{\text{select}} \Rightarrow \underline{\underline{(B)}}$

Problem 5) $A = (a_3 a_2 a_1 a_0)$; $X = (x_3 x_2 x_1 x_0)$ then the seven product bits $P = (p_6 p_5 p_4 p_3 p_2 p_1 p_0)$ can be obtained as follows:

	a_3	a_2	a_1	a_0
	x_3	x_2	x_1	x_0
	<hr/>			
	$a_3 x_0$	$a_2 x_0$	$a_1 x_0$	$a_0 x_0$
	$a_3 x_1$	$a_2 x_1$	$a_1 x_1$	$a_0 x_1$
	$a_3 x_2$	$a_2 x_2$	$a_1 x_2$	$a_0 x_2$
	$a_3 x_3$	$a_2 x_3$	$a_1 x_3$	$a_0 x_3$
	<hr/>			
p_6	p_5	p_4	p_3	p_2
p_1	p_0			

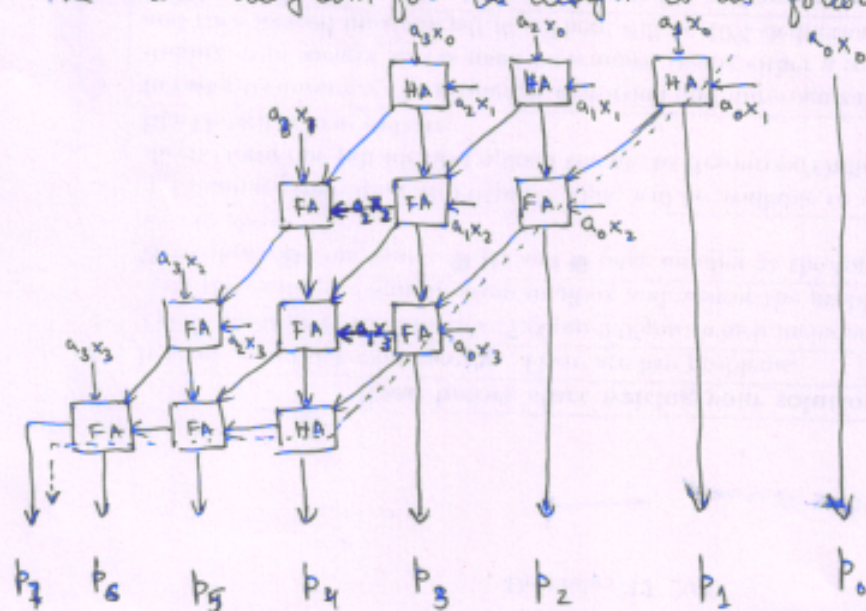The block diagram for the design is as follows.



No. of FA's required = 8

No. of HA's required = 4

Time delay of multiplier = Time delay to generate partial products + Time delay for the ~~array multiplier~~ partial products addition

$$= 1 \Delta_G + (1 \Delta_G + 2 \Delta_G + 2 \Delta_G + 1 \Delta_G + 2 \Delta_G + 2 \Delta_G)$$

$$= 11 \Delta_G$$