

## Chapter 6. High-Speed Multiplication

### 6.1. Introduction

A multiplication operation can be further divided into two steps

Step 1. Generation of partial products;

Step 2. Accumulation of the partial products.

Therefore, in order to have high-speed multiplication, we need to speedup either or both of the steps.

Lets look at the following multiplication example of  $13_{10} \times 15_{10} = (1101)_2 \times (1111)_2$ .

$$\begin{array}{r}
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \times \phantom{1} \phantom{1} \phantom{0} \phantom{1} \\
 \hline
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 + \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \hline
 1 \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1}
 \end{array}$$

The first step of the multiplication generates 4 partial products, and then the following accumulation step performs 3 two-operand addition or one four-operand addition.

Consider to convert the multiply  $15_{10} = (1111)_2$  into NAF (refer to §.6.2.1.3) using canonical recoding, then we have  $15_{10} = (1000\bar{1})_2$ . Now lets perform the multiplication as follows

$$\begin{array}{r}
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \times \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \hline
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \phantom{+} \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 + \phantom{1} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1} \\
 \hline
 1 \phantom{1} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{1} \phantom{1}
 \end{array}$$

It can be seen that the accumulation step now requires only one subtraction. In fact, reduction of the number of partial products is one effective method to enhance multiplier performance.

$$= 1 =$$

## 6.2. High-Speed Multiplier

### 6.2.1 Reducing the Number of Partial Products

1. From the fact

$$\text{Product} = \text{Multiplicand} \times \text{Multiplier},$$

we have

$$\# \text{ Partial products} = \# \text{ of 1's in the binary multiplier}.$$

2. An example:  $A \times X$ , where  $A = 10110$  and  $X = 11111$
3. Reducing the number of partial products can be realized by reducing the number of 1's in the multiplier.
4. In the above example of  $A \times X$ , convert the multiplier  $X$  into BSD:  $X = 11111 = 10000\bar{1}$ .
  - Redo the multiplication with  $X$  in BSD form.
  - It can be seen that the partial products count is reduced from 5 to 2.

#### 6.2.1.1 Booth's Algorithm

1. Idea: to replace a sequence of consecutive 1's with a one, a minus one, and a zero-run.
2. The next step is to use the carry-out signal obtained with conditions to select the results for its neighboring bit with higher weight.
3. For example,

$$X : \quad \dots 0 0 1 1 \dots 1 1 0 0 \dots$$

$\Downarrow$

$$Y : \quad \dots 0 1 0 0 \dots 0 \bar{1} 0 0 \dots$$

$$= 2 =$$

This transformation can be proved to be correct: Assume that there are  $k$  1's in  $X$ . And let the least significant bit 1 have the weight  $2^i$ . Then  $X$  has value of

$$2^i + 2^{i+1} + \dots + 2^{i+k-1} = \sum_{j=i}^{i+k-1} 2^j = 2^{i+k} - 2^i.$$

On the other hand, the value of  $Y$  can be shown as

$$(-1) \times 2^i + 2^{i+k-1} = 2^{i+k} - 2^i.$$

So  $Y$  has the same value as  $X$ .

4. Booth's algorithm can be summarized into a table form:

| $x_i$ | $x_{i-1}$ | $y_i$     |
|-------|-----------|-----------|
| 0     | 0         | 0         |
| 0     | 1         | 1         |
| 1     | 0         | $\bar{1}$ |
| 1     | 1         | 0         |

- In the table,  $x_{i-1}$  serves as a reference bit.
- To convert a binary number  $X = (x_{n-1}x_{n-2} \dots x_0)$  into Booth form, we can follow the above table by letting  $i = 0, 1, \dots, n$ .
- We always assume that  $x_{-1} = 0$  in Booth's algorithm.
- Note that this table is a parallel algorithm where we can start recoding for all values of  $i$  at the same time.
- The worst case scenario: Booth's algorithm does not always reduce the count of 1's. (show with an example:  $X = 10101$ )
- Question: If we convert an  $n$ -bit binary number into Booth form, what is the average number of nonzeros (1 or  $\bar{1}$ ) in the result?

### 6.2.1.2 Two-Bit Booth's Algorithm

1. An improvement to Booth's algorithm with reduced average number of 1's.
2. Instead of checking two bits  $x_i x_{i-1}$  to generate one digit  $y_i$ , 2-bit Booth's algorithm each time generates two digits by examining three bits. This strategy will eliminate the inefficiency of Booth's method for the case of the isolated 1's.

$$= 3 =$$

3. Two-bit Booth's algorithm can be summarized into the following table:

| $x_{i+1}$ | $x_i$ | $x_{i-1}$ | $y_{i+1}$ | $y_i$     | Operation |
|-----------|-------|-----------|-----------|-----------|-----------|
| 0         | 0     | 0         | 0         | 0         | +0        |
| 0         | 1     | 0         | 0         | 1         | +A        |
| 1         | 0     | 0         | $\bar{1}$ | 0         | -2A       |
| 1         | 1     | 0         | 0         | $\bar{1}$ | -A        |
| 0         | 0     | 1         | 0         | 1         | +A        |
| 0         | 1     | 1         | 1         | 0         | +2A       |
| 1         | 0     | 1         | 0         | $\bar{1}$ | -A        |
| 1         | 1     | 1         | 0         | 0         | +0        |

- This algorithm is also called Radix-4 Booth's Algorithm.
- In the table,  $x_{i-1}$  serves as a reference bit.
- To convert a binary number  $X = (x_{n-1}x_{n-2} \cdots x_0)$ , one can follow the above table by letting  $i = 0, 1, \dots, n$ . Note that we assume that  $x_{-1} = 0$ .
- This table is also a parallel algorithm where we can start recoding for the input bits in parallel, or start from either end of the binary number.
- The worst case scenario: Two-bit Booth's is better than Booth's, but it still does not always reduce the count of 1's. (show with an example:  $X_1 = 10101$  and  $X_2 = 101010$ )
- Question: If we convert an  $n$ -bit binary number into two-bit Booth form, what is the average number of nonzeros (1 or  $\bar{1}$ ) in the result?

### 6.2.1.3 Canonical Recoding

1. Is there a recoding algorithm that generates a BSD form with nonzeros count always less than or equal to the that of the binary input?
2. Minimal weight SD form: The number of nonzero digits in an SD form is the minimal. (show this concept with an example)
3. Non-adjacent form (NAF): An SD form where there is no two consecutive nonzero digits. Note that NAF is a special case of minimal weight SD form. (show this concept with an example)

4. Canonical recoding algorithm can convert a binary input into its NAF, which can be summarized into the following table:

| $x_{i+1}$ | $x_i$ | $c_i$ | $y_i$     | $c_{i+1}$ |
|-----------|-------|-------|-----------|-----------|
| 0         | 0     | 0     | 0         | 0         |
| 0         | 1     | 0     | 1         | 0         |
| 1         | 0     | 0     | 0         | 0         |
| 1         | 1     | 0     | $\bar{1}$ | 1         |
| 0         | 0     | 1     | 1         | 0         |
| 0         | 1     | 1     | 0         | 1         |
| 1         | 0     | 1     | $\bar{1}$ | 1         |
| 1         | 1     | 1     | 0         | 1         |

- In the table,  $c_i$  serves a similar role as a carry in addition operation.
- To convert a binary number  $X = (x_{n-1}x_{n-2} \cdots x_0)$ , one can follow the above table by letting  $i = 0, 1, \dots, n$ . Note that we assume that  $c_0 = 0$ .
- Is this a sequential algorithm or a parallel algorithm?
- The worst case scenario: The resultant BSD has the same number of nonzero digits as in the binary input.
- Question: If we convert an  $n$ -bit binary number into NAF using Canonical recoding, what is the average number of nonzeros (1 or  $\bar{1}$ ) in the result?
  - Hamming weight: The number of nonzero digits in a sequence.
  - The average Hamming weight of an  $n$ -bit binary number is  $n/2$ .
  - The average Hamming weight of an  $n$ -digit NAF is  $n/3$ .

### 6.2.2 Accumulating Partial Products

Consider  $(n\text{-bit}) \times (n\text{-bit})$  multiplication, where we let multiplicand and multiplier be  $A = (a_{n-1} \cdots a_0)$  and  $X = (x_{n-1} \cdots x_0)$ , respectively. Let  $P$  denote the product of  $A$  and  $X$ . Since  $0 \leq A, X \leq 2^n - 1$ , product  $P = (p_{2n-1} \cdots p_0)$  has up to  $2n$  bits. This can be seen as follows:


$$\begin{aligned}
 P &= A \times X \\
 &\leq (2^n - 1)(2^n - 1) \\
 &= 2^{2n} - 2^{n+1} + 1 \\
 &\leq 2^{2n} - 1.
 \end{aligned}$$

= 5 =


Lets take an example of  $(4\text{-bit}) \times (4\text{-bit})$  multiplier, where  $A = (a_3a_2a_1a_0)$  and  $X = (x_3x_2x_1x_0)$ . Then the ten product bits  $P = (p_7p_6 \cdots p_0)$  can be obtained with the scheme given below:

|       |          |          |          |          |          |          |          |
|-------|----------|----------|----------|----------|----------|----------|----------|
|       |          |          |          | $a_3$    | $a_2$    | $a_1$    | $a_0$    |
|       |          |          |          | $x_3$    | $x_2$    | $x_1$    | $x_0$    |
| <hr/> |          |          |          |          |          |          |          |
|       |          |          |          | $a_3x_0$ | $a_2x_0$ | $a_1x_0$ | $a_0x_0$ |
|       |          |          | $a_3x_1$ | $a_2x_1$ | $a_1x_1$ | $a_0x_1$ |          |
|       |          | $a_3x_2$ | $a_2x_2$ | $a_1x_2$ | $a_0x_2$ |          |          |
|       | $a_3x_3$ | $a_2x_3$ | $a_1x_3$ | $a_0x_3$ |          |          |          |
| <hr/> |          |          |          |          |          |          |          |
| $p_7$ | $p_6$    | $p_5$    | $p_4$    | $p_3$    | $p_2$    | $p_1$    | $p_0$    |

 1. The second step in a multiplication operation is accumulating partial products, which can be implemented using carry-save addition and carry-propagate addition.
2. Therefore, this is a task of designing efficient Carry-save adder for a class of special CSA tree.
3. Consider a multiplier of 4-bit by 4-bit.
  - (a) The first step is generation of 16 partial product bits, which requires 16 two-input AND gates and incurred one gate delay with  $\Delta_G$ .
  - (b) Denote a partial product bit with a circular-dot  $\circ$ . Then it can be seen that the CSA tree of 16 partial product bits form a triangular tree with 4 rows and the base consisting of 7 dots. By checking with the table given in the section of Carry-Save Adder in Chapter 5, we find that it requires 2 levels of CSA before the final CPA.



 (c) An alternate method has also 2 units of CSA and one unit of CPA.



4. In general, a multiplier of  $n$ -bit by  $n$ -bit will have a triangular CSA tree with  $n$  rows and a base consisting of  $2n - 1$  dots.
5. In multiplication, if the multiplier has different number of bits from the multiplicand, the CSA tree usually forms an isosceles trapezoid.



### 6.2.3 Squaring Unit (optional)

Consider squaring operation  $P = A^2$ . Let  $A$  be a 4-bit binary number. Then it follows

$$\begin{array}{r}
 \begin{array}{cccc}
 & & a_3 & a_2 & a_1 & a_0 \\
 \times & & a_3 & a_2 & a_1 & a_0 \\
 \hline
 & & a_3 a_0 & a_2 a_0 & a_1 a_0 & a_0^2 \\
 & a_3 a_1 & a_2 a_1 & a_1^2 & a_0 a_1 & \\
 & a_3 a_2 & a_2^2 & a_1 a_2 & a_0 a_2 & \\
 a_3^2 & a_2 a_3 & a_1 a_3 & a_0 a_3 & & 
 \end{array} \\
 \Downarrow \\
 \begin{array}{ccccccc}
 a_3 & a_3 a_2 & a_2 & a_3 a_0 & a_2 a_0 & a_1 a_0 & a_0 \\
 & a_2 a_3 & a_3 a_1 & a_2 a_1 & a_1 & a_0 a_1 & \\
 & & a_1 a_3 & a_1 a_2 & a_0 a_2 & & \\
 & & & a_0 a_3 & & & 
 \end{array} \\
 \Downarrow \\
 \begin{array}{ccccccc}
 a_3 & a_1 a_3 & a_2 & a_0 a_2 & a_1 & & a_0 \\
 a_2 a_3 & & a_1 a_2 & & a_0 a_1 & & \\
 & & a_0 a_3 & & & & 
 \end{array} \\
 + \\
 \hline
 p_7 \quad p_6 \quad p_5 \quad p_4 \quad p_3 \quad p_2 \quad p_1 \quad p_0
 \end{array}$$

Note that  $a_1 + a_0 a_1 = a_1(\overline{a_0} + a_0) + a_0 a_1 = 2a_0 a_1 + \overline{a_0} a_1$ .

### 6.3. Array Multipliers

We consider  $(5\text{-bit}) \times (5\text{-bit})$  multiplier, where  $A = (a_4a_3a_2a_1a_0)$  and  $X = (x_4x_3x_2x_1x_0)$ . Then the ten product bits  $P = (p_9p_8 \cdots p_0)$  can be obtained with the scheme given below:

|       |          |          |          |          |          |          |          |          |          |
|-------|----------|----------|----------|----------|----------|----------|----------|----------|----------|
|       |          |          |          |          | $a_4$    | $a_3$    | $a_2$    | $a_1$    | $a_0$    |
|       |          |          |          |          | $x_4$    | $x_3$    | $x_2$    | $x_1$    | $x_0$    |
|       |          |          |          |          | $a_4x_0$ | $a_3x_0$ | $a_2x_0$ | $a_1x_0$ | $a_0x_0$ |
|       |          |          |          | $a_4x_1$ | $a_3x_1$ | $a_2x_1$ | $a_1x_1$ | $a_0x_1$ |          |
|       |          | $a_4x_2$ | $a_3x_2$ | $a_2x_2$ | $a_1x_2$ | $a_0x_2$ |          |          |          |
|       | $a_4x_3$ | $a_3x_3$ | $a_2x_3$ | $a_1x_3$ | $a_0x_3$ |          |          |          |          |
| +     | $a_4x_4$ | $a_3x_4$ | $a_2x_4$ | $a_1x_4$ | $a_0x_4$ |          |          |          |          |
| $p_9$ | $p_8$    | $p_7$    | $p_6$    | $p_5$    | $p_4$    | $p_3$    | $p_2$    | $p_1$    | $p_0$    |

Assume all the partial product bits  $a_ix_j, i, j = 0, \dots, 4$ , have been generated, an array architecture to realize the above multiplication scheme using full adder as cell can be given as

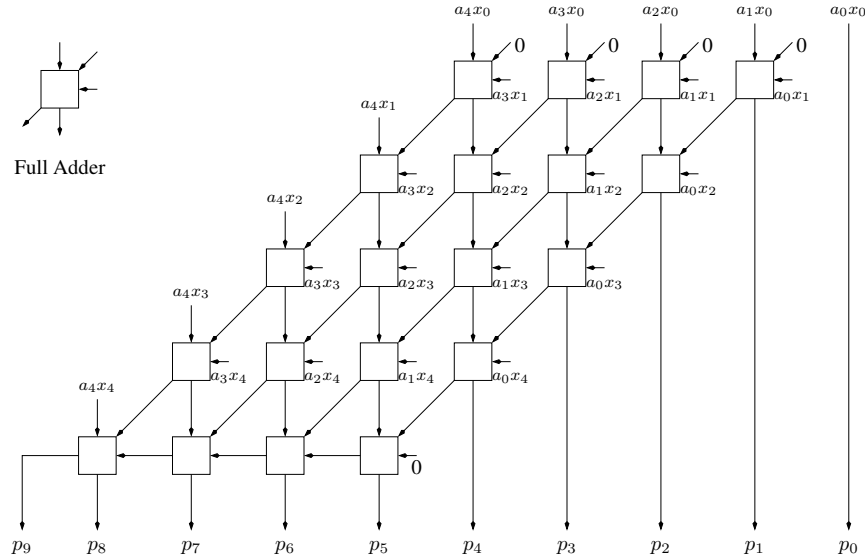


Figure 1: A  $5\text{-bit} \times 5\text{-bit}$  array multiplier using full adder as building block.

It can be seen that 20 cells or full adders are used. There are 5 cells can be replaced with half adders since one of their inputs is constant zero. A critical path can be easily found with six full adders and two half adders. A summary of the array multiplier complexities can be given as follows.

$$= 10 =$$

Note that the time delay of one full adder is two  $\Delta_G$  and one half adder is one  $\Delta_G$ .

$$\begin{cases} \text{Space complexity:} & 15\text{FAs} + 5\text{HAs} \\ \text{Time complexity:} & 6\Delta_{\text{FA}} + 2\Delta_{\text{HA}} = 14\Delta_G \end{cases}$$

## 6.4. Building Large Multiplier Using Small Multipliers

1. Consider to build a  $2n \times 2n$  multiplier by using  $n \times n$  multipliers. Let both the multiplicand  $A$  and the multiplier  $X$  be  $2n$ -bit numbers,

$$\begin{cases} A &= A_H \cdot 2^n + A_L, \\ X &= X_H \cdot 2^n + X_L, \end{cases}$$

where  $A_H, A_L, X_H, X_L$  are  $n$ -bit numbers.

2. Then it follows

$$A \cdot X = (A_H 2^n + A_L) \times (X_H 2^n + X_L) = \underbrace{A_H X_H}_1 2^{2n} + \underbrace{(A_H X_L + A_L X_H)}_2 2^n + \underbrace{A_L X_L}_4.$$

Clearly, such a  $2n \times 2n$  multiplication can be implemented with 4  $n \times n$  multipliers along with some adders.

3. Note that a  $n \times n$  multiplier yields  $2n$ -bit product. The above equation can be realized with a CSA tree of three rows and width of  $4n$ -bit.
  - Such a carry-save adder requires one unit of CSA and one unit of CPA.
  - The CSA unit uses  $2n$  FAs with a delay of  $2\Delta_G$ .
  - The CPA unit uses  $(2n - 1)$  FAs and  $n$  HAs with a time delay of  $(2(2n - 1) + n)\Delta_G = (5n - 2)\Delta_G$ .
  - The complexities of this carry save adder can be estimated as
    - $C = (4n - 1)\text{FAs} + n\text{HAs}$ .
    - $T = 5n\Delta_G$ .
4. The complexities of the  $2n \times 2n$  multiplier can now be estimated as
  - $C = 4C_{n \times n \text{ multiplier}} + (4n - 1)\text{FAs} + n\text{HAs}$ .

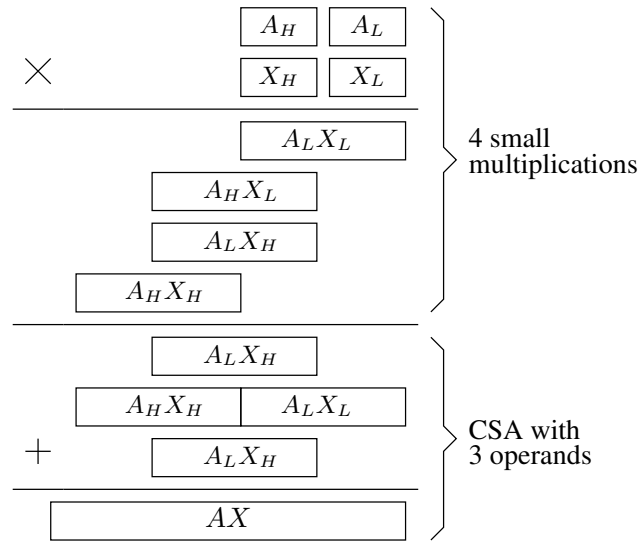


Figure 2: Multiplier built with small multipliers.

- $T = T_{n \times n \text{ multiplier}} + 5n\Delta_G.$

Note that an  $n \times n$  multiplier can be built with either methods discussed in the last two sections.