

Assignment – 4

1. (20 marks) Build a 18-bit carry-select adder. Decide the number of groups and the size of each group. Estimate the time delay of your design.

Ans.) 18-bit carry-select adder $\Rightarrow n = 18$

Let the 18-bit carry select adder be divided into L groups, each group of length k_1, k_2, \dots, k_L , then, the following inequality holds:

$$\Rightarrow 1 + (L(L-1)) / 2 \geq 18 \quad \Rightarrow L(L-1) \geq 34$$


Since, L is an integer, the minimum value of L that satisfies the above relation is $L = 7$.

Hence, the number of groups in the carry-select adder are 7.

The group size of each group would then be $k_1 = 1, k_2 = 1, k_3 = 2, k_4 = 3, k_5 = 4, k_6 = 5, k_7 = 2$

For a group l of length k_l it takes $(l-1) \times 2\Delta_G$ for its carry-in c_j signal to be available. And the latency of k_l -bit RCA is $2k_l\Delta_G$

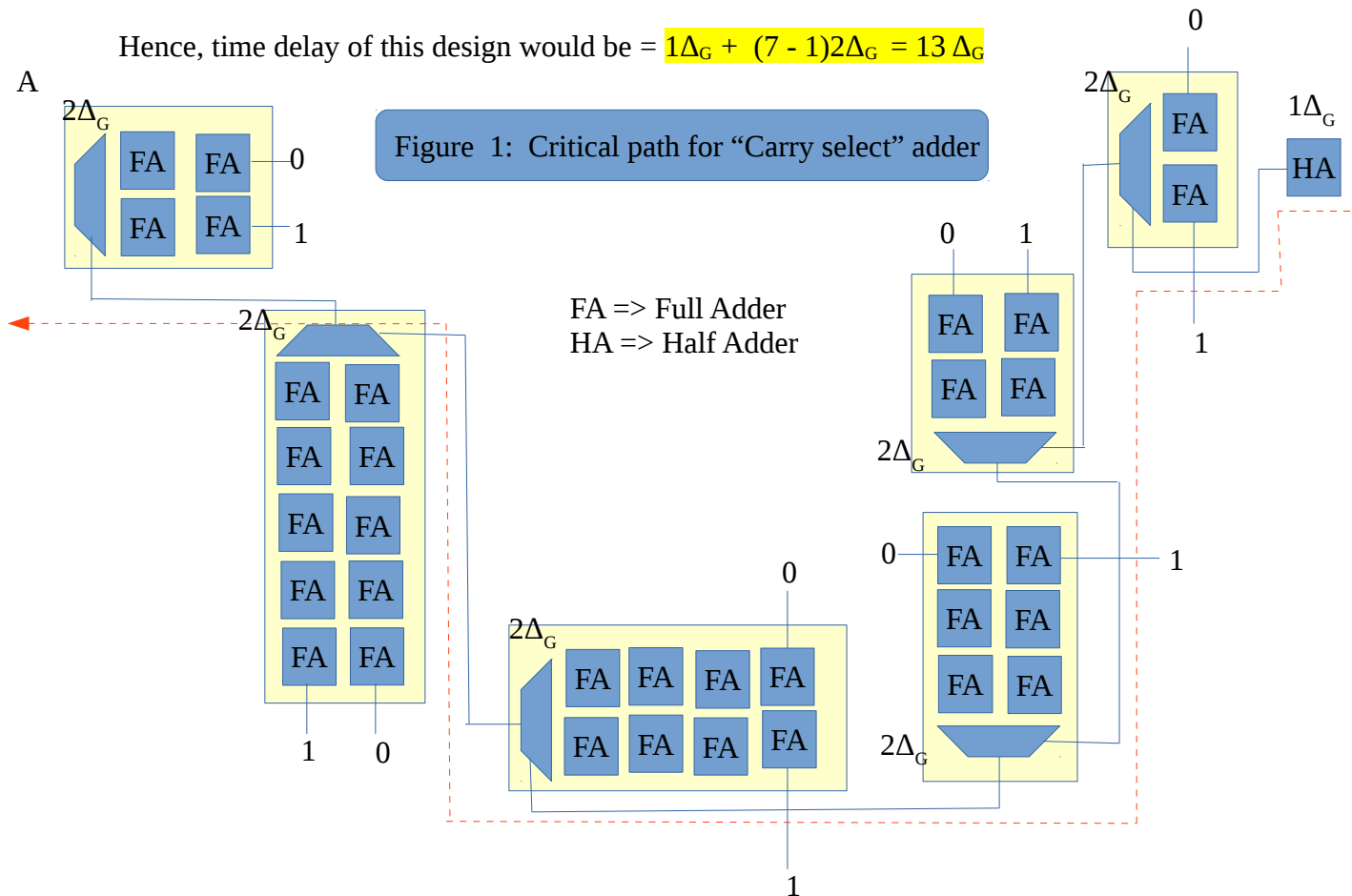Hence, time delay of this design would be $= 1\Delta_G + (7-1)2\Delta_G = 13\Delta_G$



2. (20 marks) Build a 18-bit carry-skip adder. Decide the number of groups and the size of a group. Estimate the time delay of your design.

Ans.) Let the following three time delays be defined:

t_r denote carry ripple time through one bit

$t_s(k)$ denote the time to skip on group

t_b denote the time delay of an OR gate

For a n-bit carry-skip adder, of n/k groups where k is the size of the group,

$$T_{\text{carry}} = (k - 1) t_r + t_b + (n/k - 2) (t_s + t_b) + (k - 1) t_r$$

$$= (4k + 2n/k - 7) \Delta_G$$

where $t_r = 2\Delta_G$ and $t_b = t_s = \Delta_G$

Optimal size of k $\Rightarrow k_{\text{opt}} = \sqrt{\frac{n}{2}}$

Hence, for $n = 18$, $k_{\text{opt}} = 3 \Rightarrow$ Number of groups = $n/k_{\text{opt}} = 18/3 = 6$

 


Figure 2 : Showing the critical path for “Carry Skip Adder”

\Rightarrow Size of the group = $k_{\text{opt}} = 3$

\Rightarrow Optimal time delay of the design, $T_{\text{opt}} = (4k_{\text{opt}} + 2n/k_{\text{opt}} - 7) \Delta_g$
 $= (4*3 + (2 * 18) / 3 - 7) \Delta_g = 17\Delta_g$

3. (20 marks) Build a carry-save adder that performs $X = A + B + C + D + E$, where each of operands A, B, C, D, and E has 4 bits. Draw a full diagram for the carry-save adder and estimate the complexities using both (3, 2) and (2, 2) counters as building blocks. Explicitly show a critical path.

Ans.) Since, A, B, C, D and E are 4 bit operands $\Rightarrow A, B, C, D, E \in [0, 2^4 - 1] = [0-15]$

Hence, the sum of four such numbers will have no more than $(5 \times [0-15]) \subset [0, 2^7 - 1]$ i.e. 7 bits

\Rightarrow Organize the architecture diagram in at most 7 columns.

 


Figure 3: "Carry Save Adder" using (3,2) as building blocks

The architecture complexities using only (3,2) or FA as building blocks are:

- * Circuit complexity: $C = 18(3,2)'s = 18 \text{ FA}$
- * Critical path delay: $T = 8 * (2\Delta_G) = 16 \Delta_G$

 


Figure 4: “Carry Save Adder” using (2,2) as building blocks

The architecture complexities using both (3,2) or FA and (2,2) or HA as building blocks are:

- * Circuit complexity: $C = 13(3,2)'s + 5(2,2)'s = 13 \text{ FAs} + 5 \text{ HAs}$
- * Critical path delay: $T = 6 (2\Delta_G) + 2(1\Delta_G) = 14 \Delta_G$

4. (20 marks) Consider multiplication of a 5-bit multiplicand A and a 4-bit multiplier X. Design a high-speed multiplier realizing this multiplication operation. Assume that (3, 2) and (2, 2) counters are used for carry save addition and carry-propagate addition. Show the steps in dot diagram or draw a block diagram for your design. How many (3, 2) and (2, 2) counters are required? Assume that $\Delta(3,2) = 2\Delta G$ and $\Delta(2,2) = \Delta G$. What is time delay of your multiplier?

Ans.) Let $A = (a_4a_3a_2a_1a_0)$ and $X = (x_3x_2x_1x_0)$ then the product bits $P = (p_8p_7p_6p_5p_4p_3p_2p_1p_0)$ can be obtained as follows:

				a_4	a_3	a_2	a_1	a_0
					x_3	x_2	x_1	x_0
				<hr/>				
				a_4x_0	a_3x_0	a_2x_0	a_1x_0	a_0x_0
			a_4x_1	a_3x_1	a_2x_1	a_1x_1	a_0x_1	
		a_4x_2	a_3x_2	a_2x_2	a_1x_2	a_0x_2		
	a_4x_3	a_3x_3	a_2x_3	a_1x_3	a_0x_3			
<hr/>								
p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0

* The 20 partial product bits can be generated using 20 two-input AND gates and hence requires one gate delay

 


Figure 5: Dot diagram depicting the usage of (3,2)'s and (2,2)'s for adding the partial product terms

(CPA: 4 (3,2)'s and 3 (2,2)'s)

* Let the partial product bit be denoted with a *. Then, the CSA tree of 20 partial product bits forms an isocetes trapezoid with 4 rows and base consisting of 8 asterisk's. Since, the height of the trapezoid is 4, it requires 2 levels of CSA before the final CPA.

* Number of (3,2) counter's required = 11

* Number of (2,2) counter's required = 4

 


Figure 6 : Block diagram depicting the usage of (3,2)'s and (2,2)'s for adding the partial product terms

* Time delay of the multiplier = Time to form the partial product terms (1 gate delay for the 2 input AND gates) + Time for CSA to give actual product bits (Critical path highlighted in red in Figure 6)

$$= 1 \Delta_G + (2 + 2 + 1 + 2 + 2 + 2 + 2) \Delta_G$$

$$= 14 \Delta_G$$

- * Number of Full Adder's required = 11
- * Number of Half Adder's required = 5

* **Time delay for the design** = Time to form the partial product terms (1 gate delay for the 2 input AND gates) + Time to get actual product bits (Critical path highlighted in red in Figure 7)

$$= 1 \Delta_G + (1 + 2 + 2 + 1 + 2 + 2 + 2) \Delta_G$$

$$= 13 \Delta_G$$

6. (no marks) Let a residue number system (RNS) be given by $(m_2, m_1, m_0) = (15, 14, 13)$.

(a) Solve dynamic range for the RNS.

(b) Find the RNS representations for $A = 19_{10}$ and $B = 22_{10}$. Perform $C = A \times B$ in the RNS.

(c) How many bits are required to represent a number with respect to this RNS?

Ans.)

a) Dynamic range for the RNS(15,14,13), $M = 15 * 14 * 13 = 15 * 182 = 2730$
 \Rightarrow Range = [0, 2729]

b) RNS representation for $A = 19_{10}$ is $(19 \% 15, 19 \% 14, 19 \% 13) = (4, 5, 6)$
 RNS representation for $B = 22_{10}$ is $(22 \% 15, 22 \% 14, 22 \% 13) = (7, 8, 9)$
 $C = A \times B \Rightarrow C = (4*7, 5*8, 6*9)$
 $= (28, 40, 54)$
 $= (13, 12, 2)_{\text{RNS (15,14,13)}}$

c) Bits required to represent a number w.r.t this RNS = $4 + 4 + 4 = 12$
